

From Logical Algebra to Classical Computers

⇒ Logical / Boolean Variables are Binary T and F

- We can replace them with $F \rightarrow 0$
 $T \rightarrow 1$

- Then for example

P	Q	$P \vee Q$
T	T	T
T	F	T
F	T	T
F	F	F

⇒

P	Q	$P \vee Q$
1	1	1
1	0	1
0	1	1
0	0	0

George Boole
 1847 Mathematical Analysis of Logic

1937 Symbolic Analysis of Relay and Switching Circuits

⇒ Gates

Logics

1840s
 Logical Algebra

20th
 Claude Shannon MIT
 Circuits can be designed to perform logical Algebra


Ancient Greece Aristotle Organon 321-323 BC

Start with:



- At discrete time intervals

either a pulse of electricity is transmitted
 or it is not transmitted

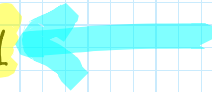Receiving
 $T \rightarrow 1$
 $F \rightarrow 0$



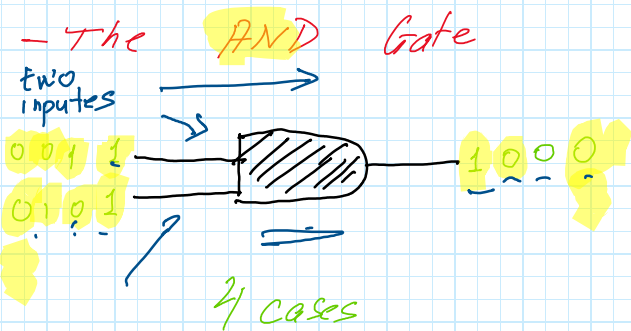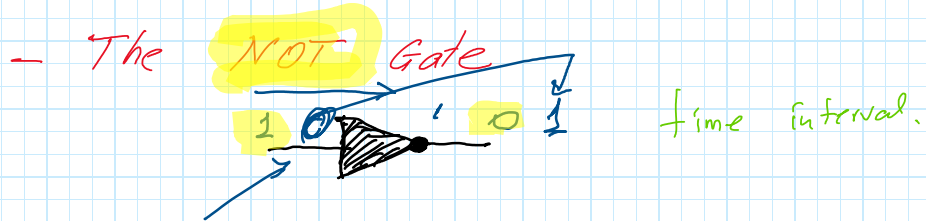- Combination of switches that corresponds to discussed logical operators - called **Gates**




- The **OR** Gate



- The **NAND** Gate



$$\neg(x \wedge y)$$

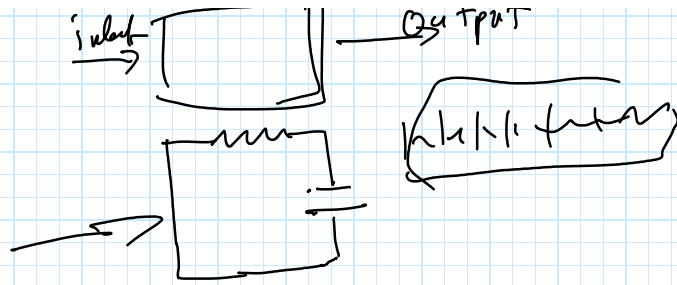


⇒ Circuits

- Connecting Gates forms a circuit
- Circuits are linear and being read from left to right
- Electrical Pulse enters from the left and being read at the right

Examples

$$\neg(\neg P \wedge \neg Q)$$

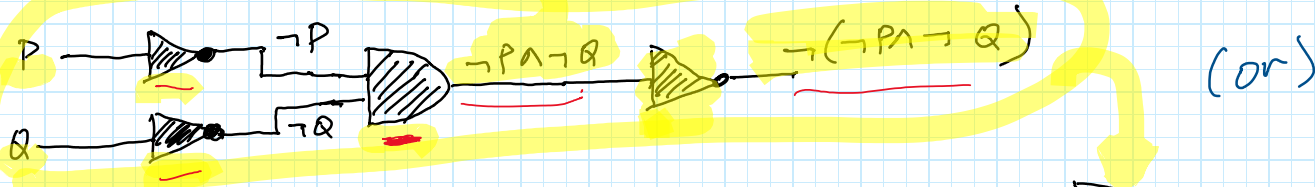

recall that $\neg(\neg P \wedge \neg Q) \equiv P \vee Q$

⇒ Gates and Computation

— Gates — fundamental building blocks of Modern Computers

— Gates — can be used to compute

— Some example

Recall exclusive or \oplus

F → 0
T → 1

P	Q	$P \oplus Q$
T	T	F
T	F	T
F	T	T
F	F	F

P	Q	$P \oplus Q$
F	F	F
F	T	T
T	F	T
T	T	F

	P	Q	$P \oplus Q$
i	0	0	0
ii	0	1	1
iii	1	0	1
iv	1	1	0

— This can be compared to adding odd and even numbers

- i even + even = even
- ii even + odd = odd

addition modulo 2

- odd + even = odd
- odd + odd = even

- ⊕ → gate is called XOR Gate



- Express through NAND

- Using this we can construct a half-adder

- half-adder - circuit adds two binary digits

- Remember Decimal half adder

if the sum < 10

2+4=6, 3+5=8 < 10

if the sum ≥ 10

7+5=12 ⇒ 7+5=2 } carry of 1
 ② → 1

$$\begin{array}{r} + 117 \\ 235 \\ \hline 352 \end{array}$$

- Binary half-adder

if the sum < 2

1+0=1, 0+0=0, 0+1=1

if the sum ≥ 2

1+1=2 ⇒ 1+1=0 } carry of 1

$$\begin{array}{r} 101 \\ 010 \\ \hline 111 \end{array}$$

101
101

1010
1 1

Ques

- schematically

101 ≡ 5

SCHEMATICALLY

1010 = 10



$0 \leftarrow 0 + 0$, carry of 0

$1 \leftarrow 0 + 1$, carry of 0

$1 \leftarrow 1 + 0$, carry of 0

$0 \leftarrow 1 + 1$, carry of 1

- Circuit

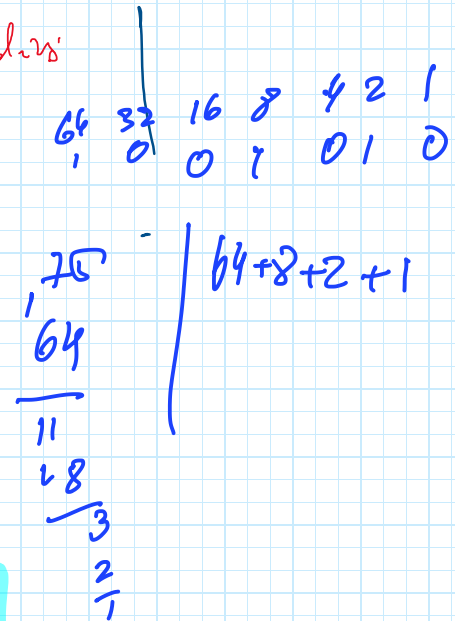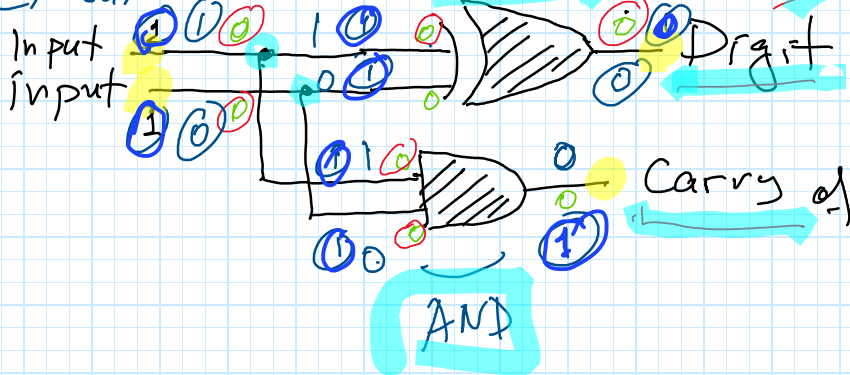

⇒ Memory

- How to store data → flip-flop

L gate with the feedback

XNAND

