

Reversible Computation
Invertible.

AND

2-inputs → 1 output

Input		Output
P	Q	
0	0	0
0	1	0
1	0	0
1	1	1

Half Adder.


Input		Output	
P	Q	digit	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

John von Neumann




information lost - energy is expended

Reversible Gates: CNOT, Toffoli, Fredkin

⇒ Controlled Not Gate → CNOT

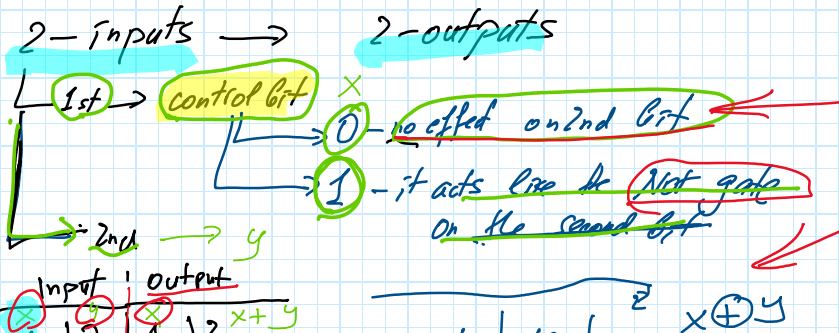

Invertible

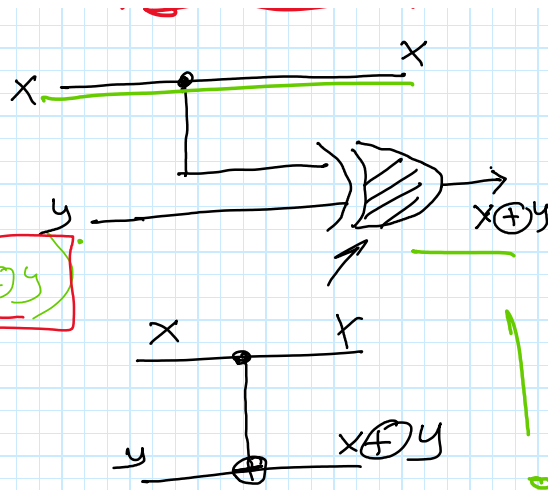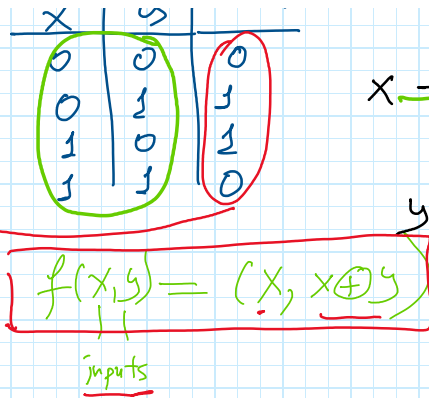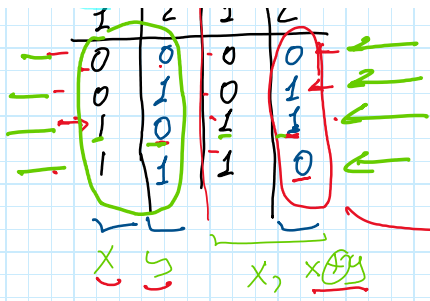

exclusive or \oplus

usual picture

CNOT is its own inverse

CNOT

Input		Output	
x	y	x	$x \oplus y$
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

CNOT

INPUT		OUTPUT	
x_1	y_1	x_1	$x_1 \oplus y_1$
0	0	0	0
0	1	0	1
1	1	1	0
1	0	1	1

logical Tables

CNOT is its own inverse

$$CNOT \cdot CNOT = I$$


$$\Rightarrow (x, y) \xrightarrow{CNOT} f(x, y) = (x, x \oplus y)$$

$$\xrightarrow{CNOT} f(x, x \oplus y) = f(x, x \oplus (x \oplus y)) = (x, y)$$

$$x \oplus x \oplus y = y \Rightarrow$$

Using the Fact That $x \oplus x = 0$ $0 \oplus y = y$

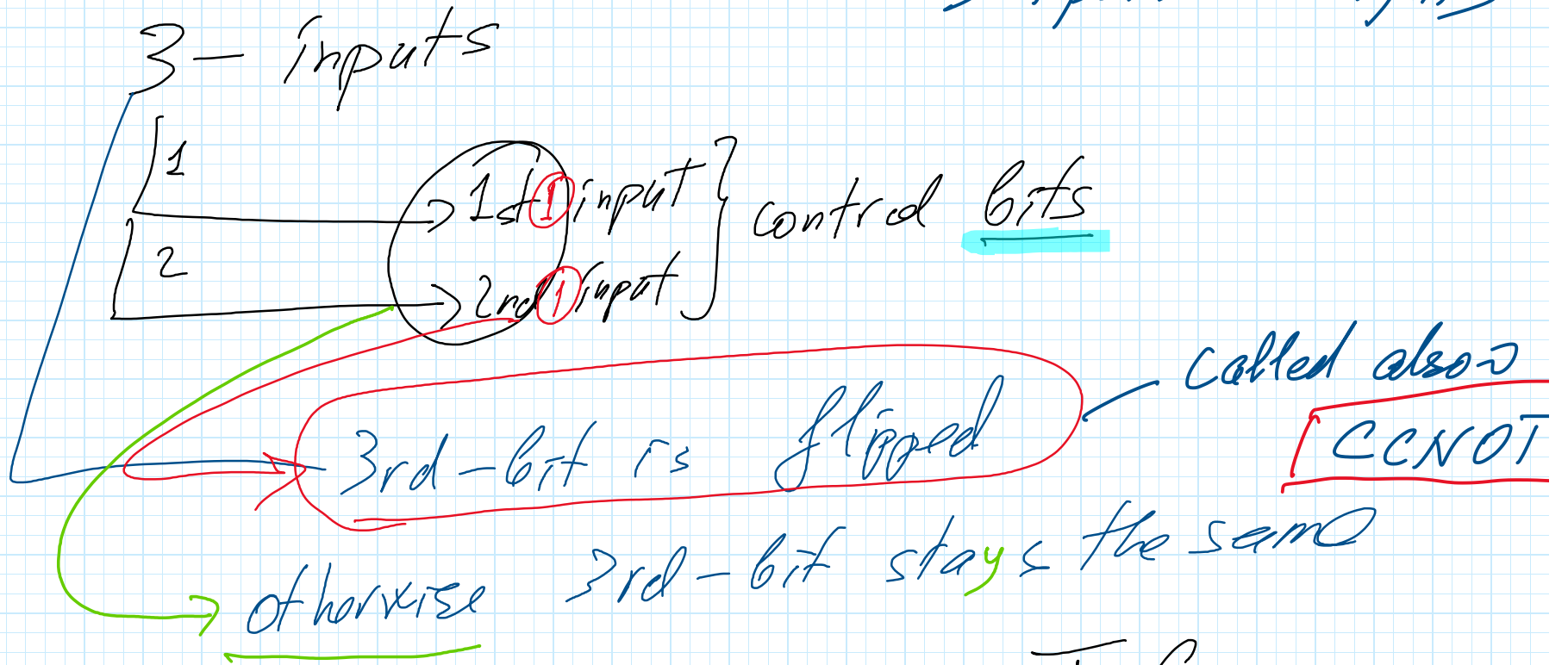
\Rightarrow The Toffoli Gate: Tommaso Toffi
3-inputs 3 outputs



Input	output
1, 1, 1	1, 1, 1
1, 1, 0	1, 1, 0
1, 0, 1	1, 0, 0
1, 0, 0	1, 0, 0
0, 1, 1	0, 1, 1
0, 1, 0	0, 1, 0
0, 0, 1	0, 0, 1
0, 0, 0	0, 0, 0

TG

Input	output
1, 1, 1	1, 1, 1
1, 1, 0	1, 1, 0
1, 0, 1	1, 0, 0
1, 0, 0	1, 0, 0
0, 1, 1	0, 1, 1
0, 1, 0	0, 1, 0
0, 0, 1	0, 0, 1
0, 0, 0	0, 0, 0


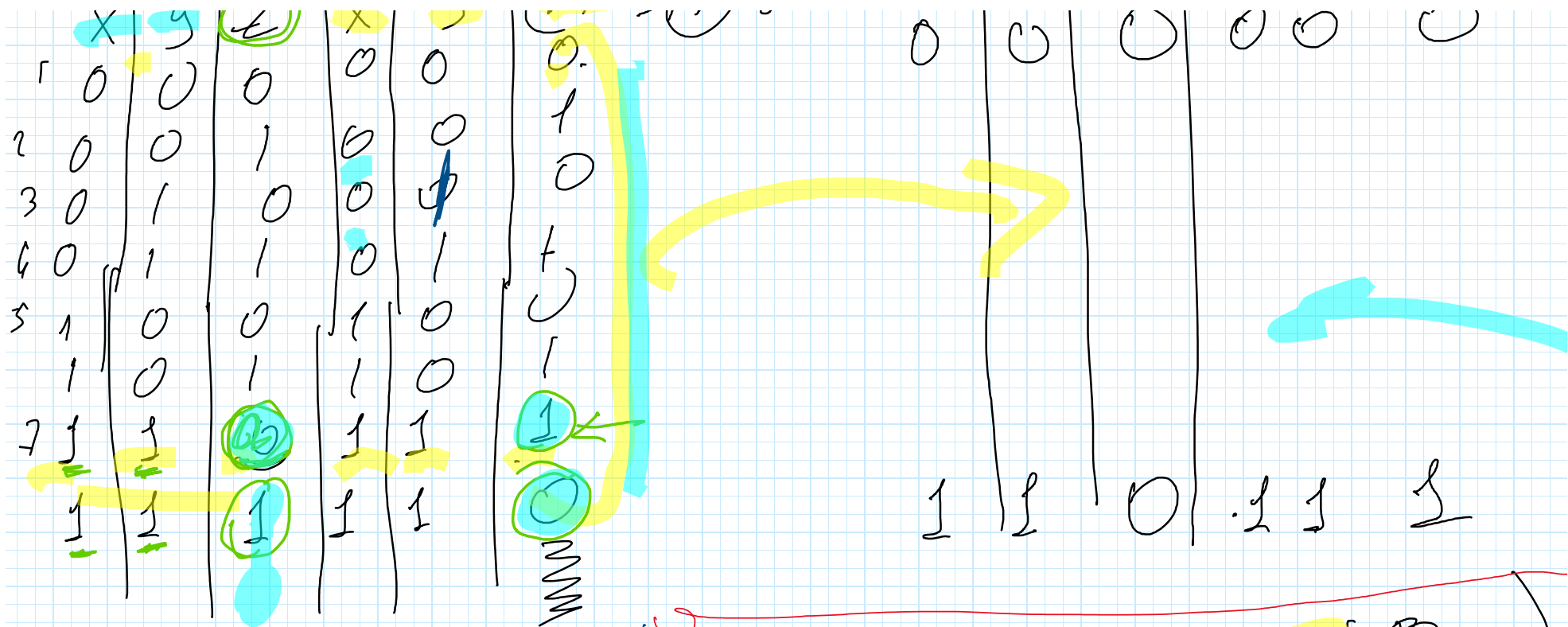


$$T(x, y, z) = (x, y, (x \wedge y) \oplus z)$$

$$(x, y, z) \rightarrow T(x, y, (x \wedge y) \oplus z) = (x, y, z)$$


$$(x, y) \oplus (x, y)$$

using

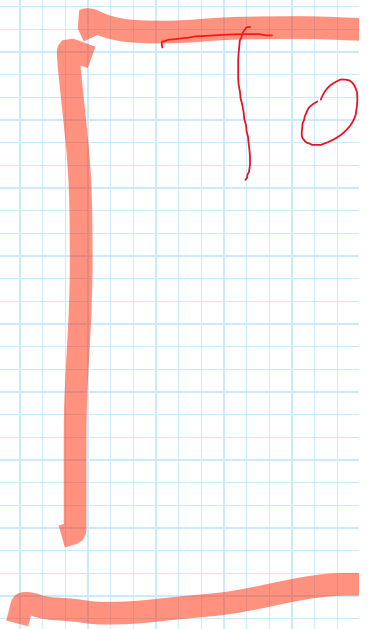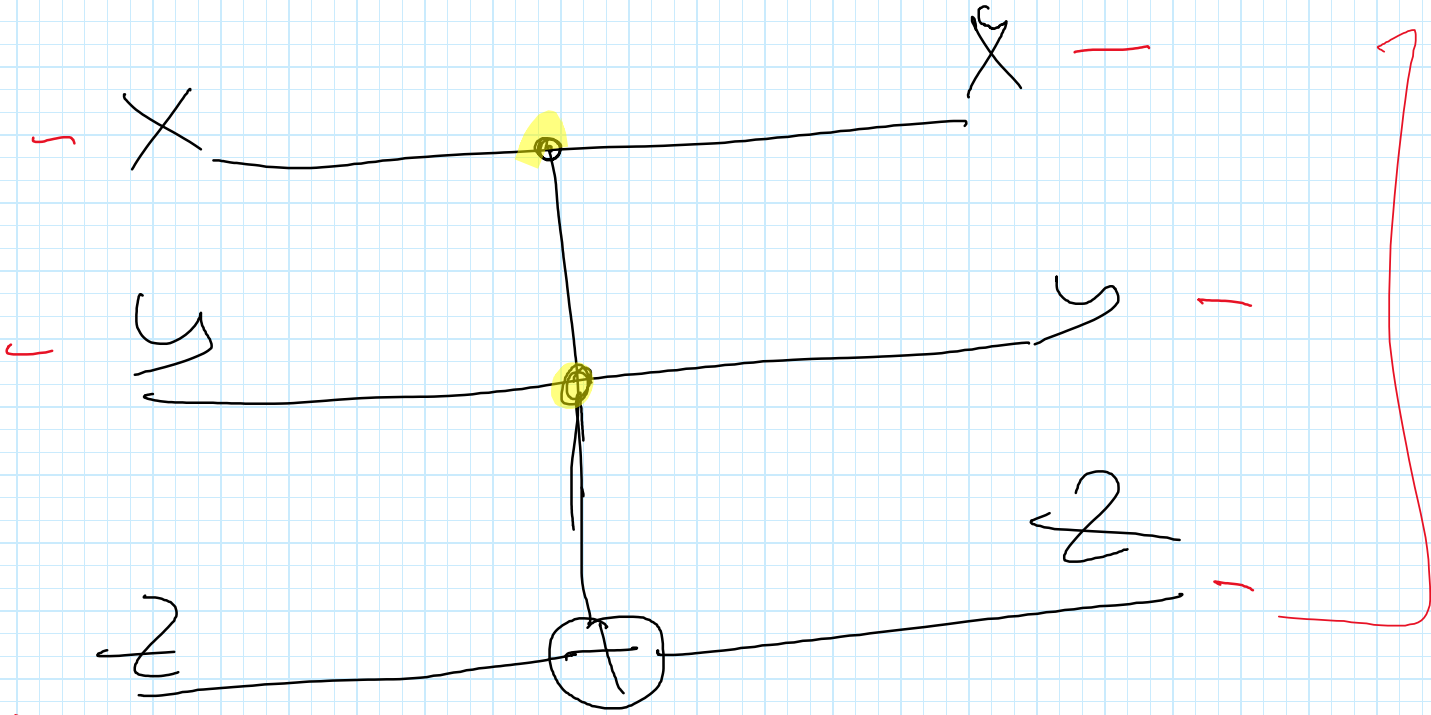

NAND

$$f(x, s) =$$

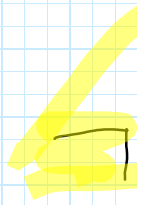


$$\neg(x \wedge y) \equiv (x \wedge y) \wedge \neg(0 \wedge 0)$$

$$\neg 0 \wedge 1$$

always z

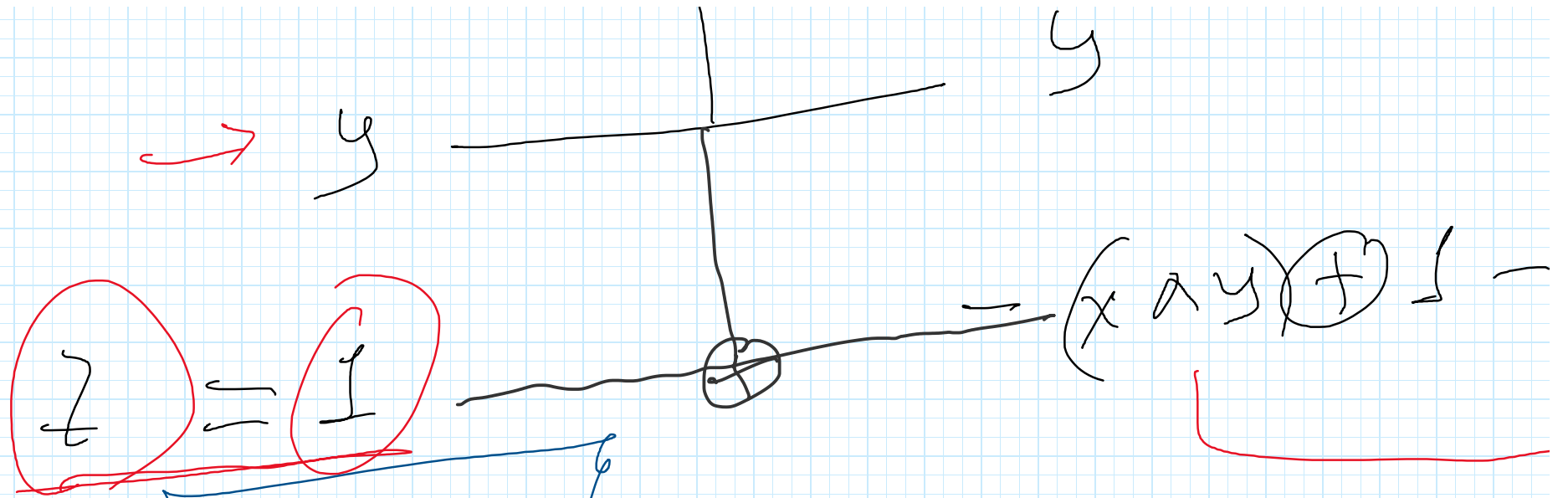
$$\neg(x, y, 1) \equiv (x, y, (x, y, 1))$$





Ancilla

Fan out

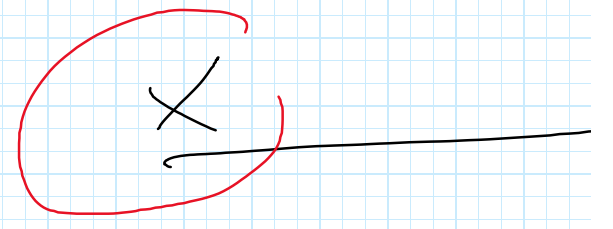


\downarrow
1 0

$$\underline{T(x, y, z)} = \underline{(x, y)}$$

$$T(X, \underline{1}, \underline{0}) = (X, \underline{1})$$

$$\frac{(X \wedge \underline{1}) \oplus \underline{0}}{(\underline{0} \wedge \underline{1}) \oplus \underline{0}} =$$
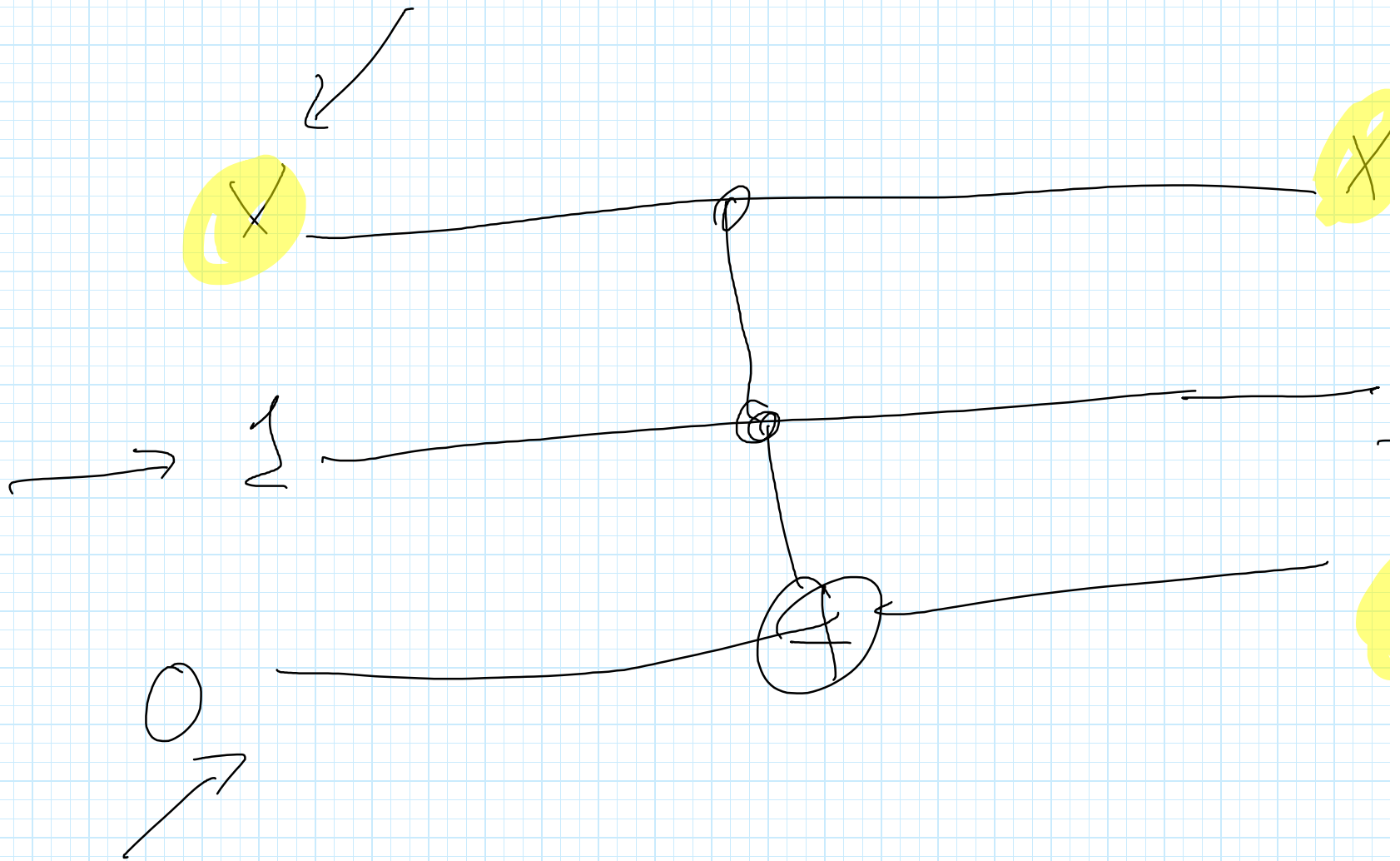
$$\frac{\cancel{(\underline{1} \wedge \underline{1})}}{\underline{1} \oplus \underline{0}} =$$



Any Boolean circuit

using just 'lof' gate

ancilla bits

garbage bits

