

Homework 7

1. (50 points) Demonstrate the logical equivalence of OR and XOR operators with $\neg(\neg P \wedge \neg Q)$

2. (50 points) Relate NOT and AND operators to NAND operator

3. (50 points) Draw circuit for $\neg(\neg P \wedge \neg Q)$, for $(P \uparrow P)$ and $(P \uparrow Q) \uparrow (P \uparrow Q)$

4. (50 points) Draw circuits for $1 + 1 = 0$ - as well as for memory unit give an explanation, how they work