

## Homework 8

1. (50 points) Show that CNOT gate is its own inverse

2. (100 points) Show that Toffoli gate is its own inverse and also is a universal gate.

- How to use Toffoli gate to make a fan - out?

3. (150 points) Show that Fredkin gate is its own inverse and also is a universal gate.

- How to use Fredkin gate to make a fan - out
- Create NAND using Fredkin and CNOT gates.